
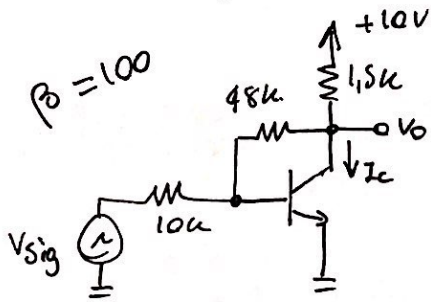


Resolução Exercício I - CEA

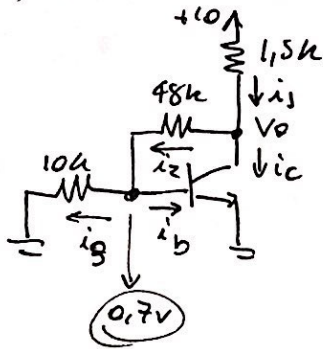

- a) calcular V_o e I_c
 b) calcular $A_v = V_o/V_{sig}$

→ a) Fazer a análise c.c.:



$$\text{LKC: } \left. \begin{aligned} i_1 &= i_c + i_2 \\ i_2 &= i_b + i_3 \end{aligned} \right\} \begin{aligned} i_1 &= \frac{10 - V_o}{1.5k} \\ i_2 &= \frac{V_o - 0.7}{48k} \\ i_3 &= \frac{0.7}{10k} \\ i_b &= i_c / \beta \end{aligned}$$

• $i_c = i_1 - i_2$
 $i_c = \beta(i_2 - i_3)$

• $i_1 - i_2 - \beta i_2 + \beta i_3 = 0$

$i_1 - (\beta + 1)i_2 + \beta i_3 = 0$

$$\frac{10 - V_o}{1.5k} - \left[\frac{(\beta + 1)V_o - (\beta + 1)0.7}{48k} \right] + \frac{\beta \cdot 0.7}{10k} = 0$$

$$\frac{10}{1.5k} + 0.7 \left[\frac{\beta + 1}{48k} + \frac{\beta}{10k} \right] = \frac{V_o}{1.5k} \left(\frac{1}{1.5k} + \frac{\beta + 1}{48k} \right)$$

$$V_o = 360.9 \times [6.67 \times 10^{-3} + 8.473 \times 10^{-3}]$$


$V_o = 5.465 \text{ V}$

→ $I_c = \frac{10 - V_o}{1.5k} - \frac{V_o - 0.7}{48k} \Rightarrow I_c = 2.924 \text{ mA}$

$$b) \quad g_m = \frac{2,924 \text{ mA}}{25 \text{ mV}} = 0,117 \text{ A/V}$$

$$r_{\pi} = \frac{V_T}{I_C} \cdot \beta = 855 \Omega$$

→ Fazendo a análise CA :

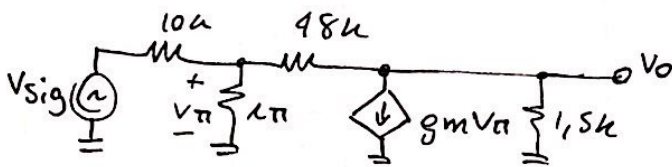

$$\text{Nós: } \left\{ \begin{array}{l} \frac{v_{sig} - v_{\pi}}{10k} = \frac{v_{\pi}}{1k} + \frac{v_{\pi} - v_o}{48k} \\ \frac{v_{\pi} - v_o}{48k} = g_m v_{\pi} + \frac{v_o}{1,5k} \end{array} \right.$$

$$\bullet \quad \frac{v_{\pi}}{48k} - g_m v_{\pi} = v_o \left(\frac{1}{1,5k} + \frac{1}{48k} \right) \Rightarrow \underline{v_o = -170,15 \cdot v_{\pi}}$$

$$\frac{v_{sig} - v_{\pi}}{10k} = \frac{v_{\pi}}{1k} + \frac{v_{\pi} - (-170,15 v_{\pi})}{48k}$$

$$v_{\pi} \left(\frac{1}{10k} + \frac{1}{1k} + \frac{1 + 170,15}{48k} \right) = \frac{v_{sig}}{10k}$$

$$\underline{v_{\pi} = 0,021 \cdot v_{sig}} \quad \longrightarrow \quad A_v = -170,15 \cdot 0,021$$

$$\boxed{A_v = -3,57 \text{ V/V}}$$